

Department of Computer Engineering
Faculty of Engineering, University of Peradeniya

C0221: Digital Design | Lab 02

Date - 25/06/2019

1. Connect the integrated circuits packages containing following gates on a breadboard and verify the functionality of them by comparing with the truth table.
 - a) NOT gate (Inverter)
 - b) 2 input OR gate
 - c) 2 input NAND gate

2. A room has two switches A and B to light a bulb. If B is closed while A is open, the bulb should NOT light. If B is open and A is closed, again the bulb should NOT light. But if both A and B are closed or A and B are both open, the bulb should light. While representing switches A and B as logic variables write a Boolean equation for the circuit to light the bulb. Implement the circuit using AND, OR and NOT gates and verify the functionality using the truth table.

3. A logic circuit has to be designed to automatically light a battery operated bulb at **night** when the **main electricity supply is cut off**. Further, in any situation it should be possible to light the bulb when a certain button is pressed. The circuit has three inputs A, B, C and one output F. The representation of logic variables are as follows.
 - A = 0 : Button is not pressed
 - A = 1 : Button is pressed
 - B = 0 : Noon
 - B = 1 : Night
 - C = 0 : Main electricity supply is cut off
 - C = 1 : Main electricity supply is available

When the output $F = 0$, the bulb is off and when $F = 1$ bulb lights up.

Implement the logic only using 2-input AND, OR, NOR, NAND gates and 1-input NOT gates and verify the functionality.