 


CO221 – Digital Design

LAB 8



SR latch with NOR gates




(a) Logic diagram

S	R	Q	Q'
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$)
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$)
1	1	0	0 (forbidden)

(b) Function table

SR latch with NAND gates

 


(a) Logic diagram

S	R	Q	Q'
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$)
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$)
0	0	1	1 (forbidden)

(b) Function table


D latch

 

(a) Logic diagram

S	R	Q	Q'
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$)
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$)
0	0	1	1 (forbidden)

(b) Function table



 


(a) Logic diagram

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

(b) Function table

Graphic symbols for latches

   

Clock response in latch and flip-flop



(a) Response to positive level




(b) Positive-edge response




(c) Negative-edge response


Master–slave D flip-flop

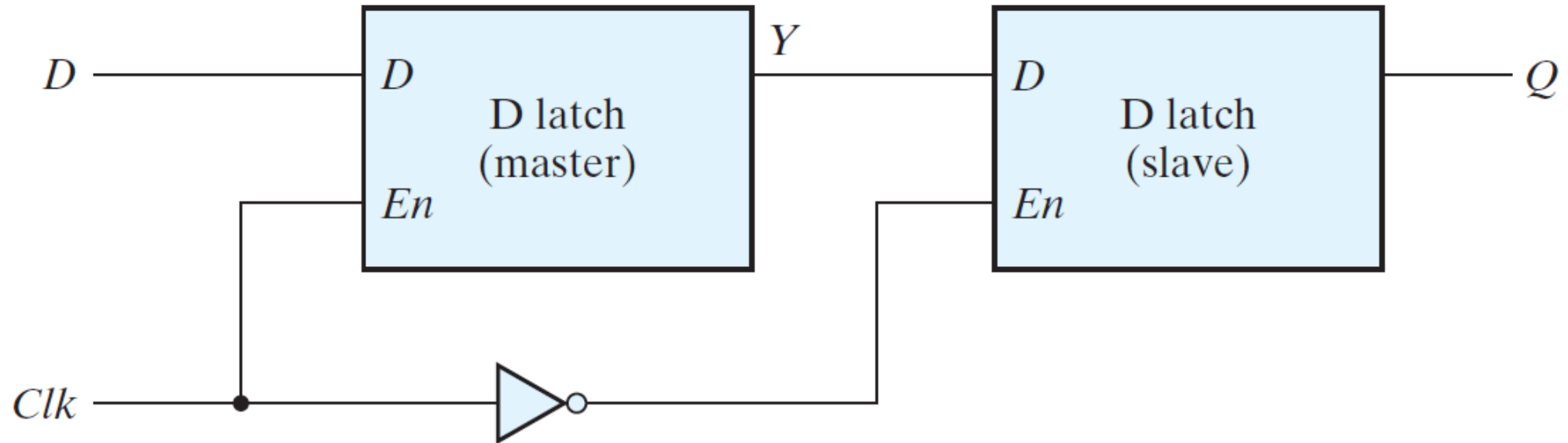

 Graphic symbol for edge-triggered D flip-flop



(a) Positive-edge

 


(a) Negative-edge


T Flip-Flop

T Flip-Flop


T	$Q(t + 1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

 

(a) From JK flip-flop

 


(b) From D flip-flop

 

(c) Graphic symbol

4-bit binary ripple counter

 

Asynchronous set and reset

